

SPIDER INDUCTIONS ELECTRONICS TASK-2

COMPONENTS:

ADC128S102

4013 Flip-Flops

LOGIC GATES (AND, NOT, OR)

L293D MOTOR DRIVE

DC MOTORS x2

SPDT Relay
(Bonus)

WORKING OF CIRCUIT:

- (i) Two pulses are sent into the the input pins (INO & INI) to show the two IR sensor inputs. The pulse associated with INO corresponds to the left sensor & INI corresponds to the right sensor.
- (ii) The Chip Select pin (CS) should be connected for ground for the ADC to work. Else, there will be high impedance in the $DOUT$ pin. Therefore, the pin is supplied with a falling edge signal that starts at $t=0s$.
- (iii) A 8 MHz Clock signal is provided to the CLK pin.
- (iv) In 4 clock ~~is~~ pulses, one complete pulse train supplied to the DIN should have gotten completed. Therefore, I have chosen the pulse width ~~of~~ of the pulse pattern signal sent to the DIN as 500 ~~ns~~ nanoseconds.

- (iv) ~~from~~ the datasheet, since we are using IN0 and IN1, ~~the~~ the pulse pattern for IN0 is chosen as 00000000 and for IN1, it is chosen as 00001000. I have taken all the DONTC ~~bits~~ (Don't care) to be zero.
- (vii) I have supplied 1.8 V to the VA pin because the threshold voltage is 1.8V and 3.3V to the VB pin because the reference voltage of the digital signal is 3.3V.
- (viii) The DOUT pin supplies a 12-bit serial data with its first six bits all being one or zero if the input from IN0 is digital high or low correspondingly and the last six ~~bits~~ bits are all one or zero corresponding ~~to~~ to the input from IN1.
- (ix) I have ~~made~~ made a 12-bit STPO Shift register from 12-flip flops connected in ~~parallel~~ ^{series} to convert the serial output from the DOUT pin to parallel output.
- (x) Using AND gates, I have ~~made~~ got two outputs in such a way that the first output is one or zero depending on the IN0 value and the second output is one or zero depending on the IN1 value.

Left	Right
0	0
0	1
1	0
1	1

→ 0 → black
 → 1 → white

IN1	IN2	IN3	IN4
0	0	0	0
0	1	1	0
1	0	0	1
1	0	1	0

→ 00 → No motion
 → 01 → backward motion
 → 10 → forward motion

(x) I have used combinational logic to get the following outputs from inputs.

WORKING OF BONUS CIRCUIT

- (i) An additional pulse input is given to IN3 pin. The IN0 corresponds to left sensor, IN1 corresponds to centre sensor and IN2 corresponds to right sensor.
- (ii) The pulse pattern ~~0000~~ supplied to DIN is changed to accommodate the IN2 pin too. At the end, the signal 00010000 is supplied to accommodate IN3 pin.
- (iii) The first 4 bits of DOUT pin corresponds to IN0, next 4 bits corresponds to IN1 and last 4 bits corresponds to IN2.
- (iv) Using combinational logic from the 12-outputs of the SPO register, 3-outputs are derived

each corresponding to the three input ~~pins~~ pin signals.

Left	Centre	Right	IN1	IN2	IN3	IN4
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	1	0	0	1
1	0	1	1	0	1	0
1	1	0	1	1	0	1
1	1	1	1	1	1	0

$IN3 \equiv \text{Right}$ & $IN4 \equiv \text{NOT}(\text{Right})$
 Except the first case where
 Left, Centre & Right are all zeros,
 $IN1 \equiv \text{Left}$ & $IN2 \equiv \text{NOT}(\text{Left})$

\therefore I ~~am~~ am using a combination of AND gates and NOT gates to determine when all the three inputs will be zero. Using a SPDT relay, I am controlling the input to the IN1 & IN2 pins for this case.